

B.Tech.
THIRD SEMESTER EXAMINATION 2015-16
EEEC302
DIGITAL ELECTRONICS

Time: 3 hours

Max Mark: 100

Note

- Attempt all questions.
- Marks and number of question to attempt from the section is mentioned before each section.
- Assume missing data suitably. Illustrate the answer with suitable sketch.

1. Attempt any four of the following:

[4x5]

- What is the difference between Binary Number and BCD number? obtain the 1's and 2's complements of the following binary numbers
 - 11101010
 - 01111110
- Subtract using 9's and 10's complement of the given numbers -
 - $(9190)_{10} - (3578)_{10}$
 - $(4566)_{10} - (6778)_{10}$
- Convert the expression $F = x' + x(x+y')(y+z')$ into standard PQS form. Also draw the logic circuit using NOR gate.
- Simplify the Boolean functions, using K-map
 $F(A,B,C,D) = \sum m(3,7,11,13,14,15)$
 Also draw the expression using only NAND gates.
- State and prove de-Morgan's first and second theorem. Convert the expression $(AB + C)(B + \bar{C}D)$ into sum of product.
- Prove that
 - $((A + \bar{B}) + AB)(A + \bar{B})(\bar{A}B) = 0$
 - $A + \bar{A}B + AB = A + B$

2. Attempt any four of the following:

[4x5]

- Draw a 32:1 Multiplexer using 4:1 Multiplexer.
- Draw the logic diagram of full adder and also derive from half adders.
- Design a BCD to 7 segment decoder using a common cathode display.
- Design a octal to binary encoder.
- Minimize the following function using Quine-McCluskey method:
 $F(A,B,C,D) = \sum m(2,4,8,9,11,15)$
- Minimize the following standard expression using K-map
 $F(A,B,C,D) = \sum m(0,1,2,6,8,10,15) + d(3,5,9,11)$

3. Attempt any two of the following:

[2x10]

- Draw and explain the master slave J-K flip flop. Explain how race around condition is avoided using master slave J-K flip-flop?

EEEC302

- What is meant by sequential circuits? Write the steps for design of asynchronous sequential machine.
 - Design and Explain the conversion from S-R flip flop in to D flip flop with truth table. Give reason why D flip flop is called as data latch?
- 4. Attempt any two of the following:** [2x10]
- Describe the difference between the following-
 - PLA and PAL
 - Static RAM and dynamic RAM
 - Classify the shift registers. Also draw and explain the circuit for serial in parallel out shift register.
 - Write short note on the following-
 - Sequence and random access memories
 - Charge coupled devices (CCD)

5. Attempt any two of the following:

[2x10]

- What do you understand by fundamental mode of operation in Asynchronous sequential circuit? Give hazard-free realization for the following Boolean function.
 $f(A,B,C,D) = \sum m(0,2,6,7,8,10,12)$
- What are the different types of hazards in asynchronous circuits? Differentiate Static-0 and Static-1 hazard with wave form.
- Explain the following:
 - Ring Counter
 - Critical race condition

OR

- For the state diagram shown in figure 1, obtain the state table and design the circuit using minimum number of J-K flip flop.

